

Electrical and Electronic Principles and Technology

JOHN BIRD, BSc(Hons) CEng CMath MIEE FIMA FIIE(ELEC) FCollP

 **Newnes**

OXFORD AUCKLAND BOSTON JOHANNESBURG MELBOURNE NEW DELHI

Contents

Preface ix

SECTION 1 Basic Electrical and Electronic Engineering Principles 1

- 1 Units associated with basic electrical quantities 3**
 - 1.1 SI units 3
 - 1.2 Charge 3
 - 1.3 Force 4
 - 1.4 Work 4
 - 1.5 Power 4
 - 1.6 Electrical potential and e.m.f. 5
 - 1.7 Resistance and conductance 5
 - 1.8 Electrical power and energy 6
 - 1.9 Summary of terms, units and their symbols 7

- 2 An introduction to electric circuits 9**
 - 2.1 Electrical/electronic system block diagrams 9
 - 2.2 Standard symbols for electrical components 10
 - 2.3 Electric current and quantity of electricity 10
 - 2.4 Potential difference and resistance 12
 - 2.5 Basic electrical measuring instruments 12
 - 2.6 Linear and non-linear devices 12
 - 2.7 Ohm's law 13
 - 2.8 Multiples and sub-multiples 13
 - 2.9 Conductors and insulators 14
 - 2.10 Electrical power and energy 15
 - 2.11 Main effects of electric current 17
 - 2.12 Fuses 18

- 3 Resistance variation 20**
 - 3.1 Resistance and resistivity 20
 - 3.2 Temperature coefficient of resistance 22
 - 3.3 Resistor colour coding and ohmic values 25

4 Chemical effects of electricity 29

- 4.1 Introduction 29
- 4.2 Electrolysis 29
- 4.3 Electroplating 30
- 4.4 The simple cell 30
- 4.5 Corrosion 31
- 4.6 E.m.f. and internal resistance of a cell 31
- 4.7 Primary cells 34
- 4.8 Secondary cells 34
- 4.9 Cell capacity 35

Assignment 1 38

5 Series and parallel networks 39

- 5.1 Series circuits 39
- 5.2 Potential divider 40
- 5.3 Parallel networks 42
- 5.4 Current division 45
- 5.5 Wiring lamps in series and in parallel 49

6 Capacitors and capacitance 52

- 6.1 Electrostatic field 52
- 6.2 Electric field strength 53
- 6.3 Capacitance 54
- 6.4 Capacitors 54
- 6.5 Electric flux density 55
- 6.6 Permittivity 55
- 6.7 The parallel plate capacitor 57
- 6.8 Capacitors connected in parallel and series 59
- 6.9 Dielectric strength 62
- 6.10 Energy stored in capacitors 63
- 6.11 Practical types of capacitor 64
- 6.12 Discharging capacitors 66

7 Magnetic circuits 68

- 7.1 Magnetic fields 68
- 7.2 Magnetic flux and flux density 69
- 7.3 Magnetomotive force and magnetic field strength 70
- 7.4 Permeability and B-H curves 70
- 7.5 Reluctance 73

- 7.6 Composite series magnetic circuits 74
- 7.7 Comparison between electrical and magnetic quantities 77
- 7.8 Hysteresis and hysteresis loss 77
- Assignment 2 81
- 8 Electromagnetism 82**
- 8.1 Magnetic field due to an electric current 82
- 8.2 Electromagnets 84
- 8.3 Force on a current-carrying conductor 85
- 8.4 Principle of operation of a simple d.c. motor 89
- 8.5 Principle of operation of a moving-coil instrument 89
- 8.6 Force on a charge 90
- 9 Electromagnetic induction 93**
- 9.1 Introduction to electromagnetic induction 93
- 9.2 Laws of electromagnetic induction 94
- 9.3 Inductance 97
- 9.4 Inductors 98
- 9.5 Energy stored 99
- 9.6 Inductance of a coil 99
- 9.7 Mutual inductance 101
- 10 Electrical measuring instruments and measurements 104**
- 10.1 Introduction 104
- 10.2 Analogue instruments 105
- 10.3 Moving-iron instrument 105
- 10.4 The moving-coil rectifier instrument 105
- 10.5 Comparison of moving-coil, moving-iron and moving-coil rectifier instruments 106
- 10.6 Shunts and multipliers 106
- 10.7 Electronic instruments 108
- 10.8 The ohmmeter 108
- 10.9 Multimeters 109
- 10.10 Wattmeters 109
- 10.11 Instrument 'loading' effect 109
- 10.12 The cathode ray oscilloscope 111
- 10.13 Waveform harmonics 114
- 10.14 Logarithmic ratios 115
- 10.15 Null method of measurement 118
- 10.16 Wheatstone bridge 118
- 10.17 D.C. potentiometer 119
- 10.18 A.C. bridges 120
- 10.19 Q-meter 121
- 10.20 Measurement errors 122
- 11 Semiconductor diodes 127**
- 11.1 Types of materials 127
- 11.2 Silicon and germanium 127
- 11.3 n-type and p-type materials 128
- 11.4 The p-n junction 129
- 11.5 Forward and reverse bias 129
- 11.6 Semiconductor diodes 130
- 11.7 Rectification 132
- 12 Transistors 136**
- 12.1 The bipolar junction transistor 136
- 12.2 Transistor action 137
- 12.3 Transistor symbols 139
- 12.4 Transistor connections 139
- 12.5 Transistor characteristics 140
- 12.6 The transistor as an amplifier 142
- 12.7 The load line 144
- 12.8 Current and voltage gains 145
- 12.9 Thermal runaway 147
- Assignment 3 152
- Formulae for basic electrical and electronic engineering principles 153
- SECTION 2 Further Electrical and Electronic Principles 155**
- 13 D.C. circuit theory 157**
- 13.1 Introduction 157
- 13.2 Kirchhoff's laws 157
- 13.3 The superposition theorem 161
- 13.4 General d.c. circuit theory 164
- 13.5 Thévenin's theorem 166
- 13.6 Constant-current source 171
- 13.7 Norton's theorem 172
- 13.8 Thévenin and Norton equivalent networks 175
- 13.9 Maximum power transfer theorem 179
- 14 Alternating voltages and currents 183**
- 14.1 Introduction 183
- 14.2 The a.c. generator 183
- 14.3 Waveforms 184
- 14.4 A.C. values 185
- 14.5 The equation of a sinusoidal waveform 189

- 14.6 Combination of waveforms 191
 14.7 Rectification 194
- Assignment 4 197
- 15 Single-phase series a.c. circuits 198**
 15.1 Purely resistive a.c. circuit 198
 15.2 Purely inductive a.c. circuit 198
 15.3 Purely capacitive a.c. circuit 199
 15.4 R - L series a.c. circuit 201
 15.5 R - C series a.c. circuit 204
 15.6 R - L - C series a.c. circuit 206
 15.7 Series resonance 209
 15.8 Q -factor 210
 15.9 Bandwidth and selectivity 212
 15.10 Power in a.c. circuits 213
 15.11 Power triangle and power factor 214
- 16 Single-phase parallel a.c. circuits 219**
 16.1 Introduction 219
 16.2 R - L parallel a.c. circuit 219
 16.3 R - C parallel a.c. circuit 220
 16.4 L - C parallel a.c. circuit 222
 16.5 LR - C parallel a.c. circuit 223
 16.6 Parallel resonance and Q -factor 226
 16.7 Power factor improvement 230
- 17 D.C. transients 236**
 17.1 Introduction 236
 17.2 Charging a capacitor 236
 17.3 Time constant for a C - R circuit 237
 17.4 Transient curves for a C - R circuit 238
 17.5 Discharging a capacitor 241
 17.6 Current growth in an L - R circuit 243
 17.7 Time constant for an L - R circuit 244
 17.8 Transient curves for an L - R circuit 244
 17.9 Current decay in an L - R circuit 245
 17.10 Switching inductive circuits 248
 17.11 The effects of time constant on a rectangular waveform 248
- 18 Operational amplifiers 252**
 18.1 Introduction to operational amplifiers 252
 18.2 Some op amp parameters 254
 18.3 Op amp inverting amplifier 255
 18.4 Op amp non-inverting amplifier 257
 18.5 Op amp voltage-follower 258
 18.6 Op amp summing amplifier 259
 18.7 Op amp voltage comparator 260
 18.8 Op amp integrator 260
 18.9 Op amp differential amplifier 262
 18.10 Digital to analogue (D/A) conversion 264
 18.11 Analogue to digital (A/D) conversion 264
- Assignment 5 269
- Formulae for further electrical and electronic engineering principles 271
- SECTION 3 Electrical Power Technology 273**
- 19 Three-phase systems 275**
 19.1 Introduction 275
 19.2 Three-phase supply 275
 19.3 Star connection 276
 19.4 Delta connection 279
 19.5 Power in three-phase systems 281
 19.6 Measurement of power in three-phase systems 283
 19.7 Comparison of star and delta connections 288
 19.8 Advantages of three-phase systems 288
- 20 Transformers 291**
 20.1 Introduction 291
 20.2 Transformer principle of operation 292
 20.3 Transformer no-load phasor diagram 294
 20.4 E.m.f. equation of a transformer 296
 20.5 Transformer on-load phasor diagram 298
 20.6 Transformer construction 299
 20.7 Equivalent circuit of a transformer 300
 20.8 Regulation of a transformer 301
 20.9 Transformer losses and efficiency 302
 20.10 Resistance matching 305
 20.11 Auto transformers 307
 20.12 Isolating transformers 309
 20.13 Three-phase transformers 309

- 20.14 Current transformers 310
- 20.15 Voltage transformers 311
- Assignment 6 315
- 21 D.C. machines 316**
 - 21.1 Introduction 316
 - 21.2 The action of a commutator 317
 - 21.3 D.C. machine construction 317
 - 21.4 Shunt, series and compound windings 318
 - 21.5 E.m.f. generated in an armature winding 318
 - 21.6 D.C. generators 320
 - 21.7 Types of d.c. generator and their characteristics 321
 - 21.8 D.C. machine losses 325
 - 21.9 Efficiency of a d.c. generator 325
 - 21.10 D.C. motors 326
 - 21.11 Torque of a d.c. motor 327
 - 21.12 Types of d.c. motor and their characteristics 329
 - 21.13 The efficiency of a d.c. motor 332
 - 21.14 D.C. motor starter 335
 - 21.15 Speed control of d.c. motors 335
 - 21.16 Motor cooling 338
- 22 Three-phase induction motors 342**
 - 22.1 Introduction 342
 - 22.2 Production of a rotating magnetic field 342
 - 22.3 Synchronous speed 344
 - 22.4 Construction of a three-phase induction motor 345
 - 22.5 Principle of operation of a three-phase induction motor 346
 - 22.6 Slip 346
 - 22.7 Rotor e.m.f. and frequency 347
 - 22.8 Rotor impedance and current 348
 - 22.9 Rotor copper loss 349
 - 22.10 Induction motor losses and efficiency 349
 - 22.11 Torque equation for an induction motor 351
 - 22.12 Induction motor torque-speed characteristics 354
 - 22.13 Starting methods for induction motors 355
 - 22.14 Advantages of squirrel-cage induction motors 355
 - 22.15 Advantages of wound rotor induction motors 356
 - 22.16 Double cage induction motor 357
 - 22.17 Uses of three-phase induction motors 357
- Assignment 7 360
- Formulae for electrical power technology 361
- Answers to multi-choice questions 363
- Index 365

Index

- Absolute permeability, 71
- Absolute permittivity, 55
- A.c. bridges, 120
 - generator, 183
 - values, 185
- Acceptor circuit, 209
- Active power, 214
- Advantages of:
 - squirrel cage induction motor, 355
 - three-phase systems, 288
 - wound rotor induction motor, 356
- Air capacitors, 64
- Alkaline cell, 35
- Alternating voltages and currents, 183
- Ammeter, 12, 106
- Amplifier gain, 255, 257
- Amplifier, transistor, 142
- Amplitude, 112, 185, 189
- Analogue instruments, 105
 - to digital conversion, 264
- Angular velocity, 189
- Anode, 29
- Apparent power, 214
- Armature, 318
 - reaction, 318
- Atoms, 10
- Attraction-type m.i. instrument, 105
- Audio frequency transformer, 299
- Auto transformer, 307
- Avalanche effect, 132
- Average value, 185
- Avometer, 12, 109

- Back e.m.f., 326
- Bandwidth, 212, 253
- Base, 136
- Battery, 32
- B-H curves, 70, 71
- Bipolar junction transistor, 136
- Block diagram, electrical, 9, 10
- Bridge, a.c., 120
 - rectifier, 132
 - Wheatstone, 118
- Brush contact loss, 325
- Buffer amplifier, 258

- Calibration accuracy, 122
- Capacitance, 54
- Capacitive a.c. circuit, 199
 - reactance, 199
- Capacitors, 54
 - charging, 236
 - discharging, 66, 241
 - energy stored, 63
 - in parallel and series, 59
 - parallel plate, 57
 - practical types, 64
- Capacity of cell, 35
- Cathode, 29
- Cathode ray oscilloscope, 12, 111
 - double beam, 112
- Cell capacity, 35
 - primary, 34
 - secondary, 34
 - simple, 30
- Ceramic capacitor, 65
- Characteristics, transistor, 140
- Charge, 3, 54
 - density, 55
 - force on, 90
- Charging a capacitor, 236
 - of cell, 32
- Chemical effects of current, 17, 18, 29
- Circuit diagram symbols, 10, 11
- Closed-loop gain, 256
- Coercive force, 78
- Collector, 136
- Colour coding of resistors, 25
- Combination of waveforms, 191
- Common-mode rejection ratio, 254
- Commutation, 317
- Commutator, 317, 318
- Comparison between electrical and magnetic quantities, 77
- Complex wave, 114
- Composite series magnetic circuits, 74
- Compound winding, 318
- Compound wound generator, 323
 - motor, 332
- Conductance, 5, 6
- Conductors, 11, 14, 127
- Constant current source, 171
- Contact potential, 129
- Continuity tester, 109
- Control, 89
- Cooling of transformers, 300
- Copper loss, 302, 325
 - rotor, 349

- Core loss, 325
 - component, 294
- Core type transformer, 299
- Corrosion, 31
- Coulomb, 3, 11
- Coulomb's law, 53
- Crest value, 185
- Current, 10
 - decay in L-R circuit, 245
 - division, 45
 - gain, transistor, 145
 - growth, L-R circuit, 243
 - main effects, 17
 - transformer, 311
- Cycle, 184

- Damping, 89, 105
- D.C. circuit theory, 157, 164
 - generator, 320
 - characteristics, 321
 - efficiency, 325
- D.C. machine, 316
 - construction, 317
 - losses, 325
 - torque, 327
- D.C. motor, 89, 326
 - efficiency, 332
 - speed control, 335
 - starter, 335
 - types, 329
- D.C. potentiometer, 119
 - transients, 236
- Decibel, 115
 - meter, 116
- Delta connection, 279
- Delta/star comparison, 288
- Depletion layer, 129
- Dielectric, 54, 56
 - strength, 62
- Differential amplifier, 260, 262
- Differentiator circuit, 248
- Digital to analogue conversion, 264
 - voltmeter, 108
- Discharging capacitors, 66, 241
 - of cell, 31
- Diverter, 336
- Doping, 128
- Double beam c.r.o., 112
- Double cage induction motor, 357
- Drift, 11
- Dynamic current gain, 144
 - resistance, 227

- Edison cell, 35
- Eddy current loss, 302
- Effective value, 185
- Effect of time constant on rectangular wave, 248
- Effects of electric current, 17
- Efficiency of:
 - d.c. generator, 325
 - d.c. motor, 332
 - induction motor, 349
 - transformer, 302, 303
- Electrical:
 - energy, 16
 - measuring instruments, 12, 104
 - potential, 5
 - power, 15
- Electric:
 - bell, 84
 - cell, 30
 - field strength, 53
 - flux density, 55
- Electrochemical series, 30
- Electrodes, 29
- Electrolysis, 29
- Electrolyte, 29, 34
- Electrolytic capacitor, 65
- Electromagnetic induction, 93
 - laws of, 94
- Electromagnetism, 82
- Electromagnets, 84
- Electronic instruments, 108
- Electrons, 10, 29
- Electroplating, 30
- Electrostatic field, 52
- E.m.f., 5
 - equation of transformer, 296
 - in armature winding, 318
 - induced in conductors, 95
 - of a cell, 31
- Emitter, 136
- Energy, 4, 16
 - stored in:
 - capacitor, 63
 - inductor, 99
- Equivalent circuit of transformer, 300

- Farad, 54
- Faraday's laws, 94
- Ferrite, 78
- Fleming's left hand rule, 86
- Fleming's right hand rule, 94
- Force, 4
 - on a charge, 90
 - current-carrying conductor, 85
- Form factor, 185
- Formulae, lists of, 153, 271, 361
- Forward bias, 129, 136
 - characteristics, 130
- Frequency, 184, 189
- Friction and windage losses, 325
- Full wave rectification, 132
- Fuses, 18

- Galvanometer, 118
 Generator:
 a.c., 183
 d.c., 316
 Germanium, 127
 Grip rule, 84
- Half-power points, 212
 Half-wave rectification, 132
 Harmonics, 114
 Heating effects of current, 17, 18
 Henry, 97
 Hertz, 184
 Hole, 128
 Hysteresis, 77
 loop, 77, 78
 loss, 78, 302
- Impedance, 201, 205
 triangle, 201, 205
 Induced e.m.f., 95
 Inductance, 97
 of a coil, 99
 Induction motor, 342
 construction, 345
 double cage, 357
 losses and efficiency, 349
 principle of operation, 346
 production of rotating field, 342
 starting methods, 355
 torque equation, 351
 -speed characteristic, 354
 uses of, 357
 Inductive a.c. circuit, 198
 switching, 248
 reactance, 198
 Inductors, 98
 Initial slope and three point method, 238
 Instantaneous values, 185
 Instrument loading effect, 109
 Insulation resistance tester, 109
 Insulators, 11, 15, 127
 Integrator circuit, 248
 op amp, 260
 Internal resistance of cell, 31
 Interpoles, 317
 Inverting amplifier op amp, 255
 Iron losses, 302, 325
 Isolating transformer, 309
- Joule, 4, 6, 16
- Kilowatt hour, 6, 16
 Kirchhoff's laws, 157
- Lamps in series and parallel, 49
 Lap winding, 318
 Laws of electromagnetic induction, 94
 L-C parallel circuit, 222
 Lead acid cell, 34
 Leclanche cell, 34
 Lenz's law, 9
 Lifting magnet, 85
 Linear device, 12
 Linear scale, 105
 Lines of electric force, 52
 Lines of magnetic flux, 68
 Load line, 144, 145
 Local action, 30
 Logarithmic ratios, 115
 Losses:
 d.c. machines, 325
 induction motors, 349
 transformers, 302
 Loudspeaker, 86
 LR-C a.c. circuit, 223
- Magnetic:
 circuits, 68, 74
 effects of current, 17, 18
 field due to electric current, 82
 fields, 68
 field strength, 70
 flux, 69
 flux density, 69
 screens, 73
 Magnetisation curves, 71
 Magnetising component, 294
 Magnetising force, 70
 Magnetomotive force, 70
 Majority carriers, 129
 Matching, 305
 Maximum power transfer theorem, 179
 value, 185, 189
 Maxwell bridge, 120
 Mean value, 185
 Measurement errors, 122
 of power in 3 phase system, 183
 Megger, 109
 Mercury cell, 34
 Mesh connection, 279
 Mica capacitor, 64
 Minority carriers, 130
 Motor cooling, 338
 d.c., 89, 316, 326
 efficiency, 332
 speed control, 335
 starter, 335
 types, 329
 Moving coil instrument, 89
 Moving coil rectifier instrument, 105
 iron instrument, 105
 Multimeter, 12, 109
 Multiples of units, 13

- Multiplier, 107
- Mutual induction, 97, 101

- Negative feedback, 253
- Neutral conductor, 276
- Neutrons, 10
- Newton, 4
- Nife cell, 35
- Non-inverting amplifier, 258
- Non-linear device, 12, 13
- n-p-n transistor, 137
- Norton's theorem, 172
 - and Thévenin equivalent circuits, 175
- n-type material, 128
- Nucleus, 10
- Null method of measurement, 118

- Ohm, 5, 12
- Ohmmeter, 12, 108
- Ohm's law, 13
- Operational amplifiers, 252
 - differential amplifier, 262
 - integrator, 260
 - inverting amplifier, 255
 - non-inverting amplifier, 257
 - parameters, 254
 - summing amplifier, 259
 - transfer characteristics, 253
 - voltage comparator, 260
 - voltage follower, 258

- Paper capacitor, 64
- Parallel:
 - a.c. circuits, 219
 - connected capacitors, 59
 - lamps, 49
 - networks, 42
 - plate capacitor, 57
 - resonance, 224, 226
- Peak factor, 186
- Peak value, 112, 185
- Peak-to-peak value, 185, 189
- Period, 184
- Periodic time, 111, 184, 189
- Permanent magnet, 68
- Permeability, 70
 - absolute, 71
 - of free space, 71
 - relative, 71
- Permittivity, 55
 - absolute, 55
 - of free space, 55
 - relative, 55
- Phasor, 189
- Plastic capacitor, 65
- Polarisation, 30

- Potential:
 - difference, 5, 12
 - divider, 40
 - gradient, 53
- Potential, electric, 5
- Potentiometer, d.c., 119
- Power, 4, 6, 15
 - active, 214
 - apparent, 214
 - factor, 214
 - improvement, 230
 - in a.c. circuits, 213
 - 3-phase systems, 281
 - measurement in 3-phase systems, 283
 - reactive, 214
 - transformers, 299
 - triangle, 214
- p-n junction, 129
- p-n-p transistor, 137
- p-type material, 128
- Practical types of capacitor, 64
- Prefixes of units, 3
- Primary cells, 34
- Principle of operation of:
 - moving-coil instrument, 89
 - d.c. motor, 89
 - 3-phase induction motor, 346
 - transformer, 292
- Protons, 10

- Q-factor, 121, 210, 227
- Q-meter, 121
- Quantity of electricity, 11

- Radio frequency transformer, 299
- Rating, 292
- R-C parallel a.c. circuit, 220
- R-C series a.c. circuit, 204
- Reactive power, 214
- Rectification, 132, 194
- Regulation of transformer, 301
- Relative permeability, 71
- Relative permittivity, 55
- Relay, 85
- Reluctance, 73
- Rejector circuit, 227
- Remanence, 78
- Repulsion type m.i. instrument, 105
- Resistance, 5, 12, 20
 - internal, 31
 - matching, 305
 - variation, 20
- Resistivity, 20
- Resistor colour coding, 25
- Resonance:
 - parallel, 224, 226
 - series, 206, 209

- Reverse bias, 130, 136
 - characteristics, 130
- R-L parallel a.c. circuit, 219
 - series a.c. circuit, 201
- R-L-C series a.c. circuit, 206
- R.m.s. value, 112, 185
- Rotor copper loss, 349

- Scale, 105
- Screw rule, 83, 84
- Secondary cells, 34
- Selectivity, 213
- Self-excited generators, 320, 321
- Self inductance, 97
- Semiconductor diodes, 127, 130
- Semiconductors, 127
- Separately-excited generators, 320, 321
- Series:
 - a.c. circuits, 198
 - circuit, 39
 - connected capacitors, 59
 - lamps, 49
 - resonance, 206, 209
 - winding, 318
 - wound generator, 323
 - motor, 331
- Shells, 10
- Shell type transformer, 299
- Shunt, 107
 - field regulator, 335
 - winding, 318
 - wound generator, 322
 - motor, 329
- Siemen, 6
- Silicon, 127
- Simple cell, 30
- Sine wave, 184, 185
- Single-phase:
 - parallel a.c. circuit, 219
 - series a.c. circuit, 198
 - voltage, 275
- Sinusoidal waveform equation, 189
- S.I. units, 3
- Slew rate, 255
- Slip, 346
- Solenoid, 83
- Speed control of d.c. motors, 335
- Squirrel-cage rotor induction motor, 345, 355
 - advantages of, 355
- Star connection, 276
- Star/delta comparison, 288
- Stator, 317
- Steady state, 237
- Sub-multiples of units, 13
- Sub-system, 10
- Summing amplifier, 259
- Superposition theorem, 161
- Switching inductive circuits, 248

- Symbols, electrical, 10, 11
- Synchronous speed, 343, 344
- System, electrical, 9

- Tangent method, 238
- Telephone receiver, 85
- Temperature coefficient of resistance, 22
- Thermal runaway, 147
- Thévenin's theorem, 166
 - and Norton equivalent circuits, 175
- Three-phase:
 - induction motor, 342
 - supply, 275
 - systems, 275
 - advantages of, 288
 - power, 281
 - transformers, 309
- Time constant:
 - CR circuit, 237, 238
 - LR circuit, 244
- Titanium oxide capacitor, 65
- Torque equation:
 - for induction motor, 351
 - of a d.c. machine, 327
 - speed characteristic of induction motor, 354
- Transformation ratio, 292
- Transformers, 291
 - auto, 307
 - construction, 299
 - current, 311
 - e.m.f. equation, 296
 - equivalent circuit, 300
 - isolating, 309
 - losses and efficiency, 302, 303
 - no-load phasor diagram, 294
 - on-load phasor diagram, 298
 - principle of operation, 292
 - regulation of, 301
 - three-phase, 309
 - voltage, 312
- Transient CR circuit, 238
- Transient LR circuit, 244
- Transistor:
 - action, 137
 - amplifier, 142
 - characteristics, 140
 - connections, 139
 - symbols, 139
- Transistors, 136
- True power, 214

- Unit of electricity, 16
- Units, 3, 7

- Variable air capacitor, 64
- Virtual earth, 255

Volt, 5, 12
Voltage, 12
 comparator, 260
 follower amplifier, 258
 gain, transistor, 146
 transformer, 312
 triangle, 201, 204
Voltmeter, 12, 107

Watt, 4, 15
Wattmeter, 109
Wave winding, 318
Waveform harmonics, 114

Waveforms, 184
 combination of, 191
Weber, 69
Wheatstone bridge, 118, 170
Work, 4
Wound rotor induction motor, 346, 355
 advantages of, 356

Yoke, 317

Zener diode, 132
Zener effect, 132